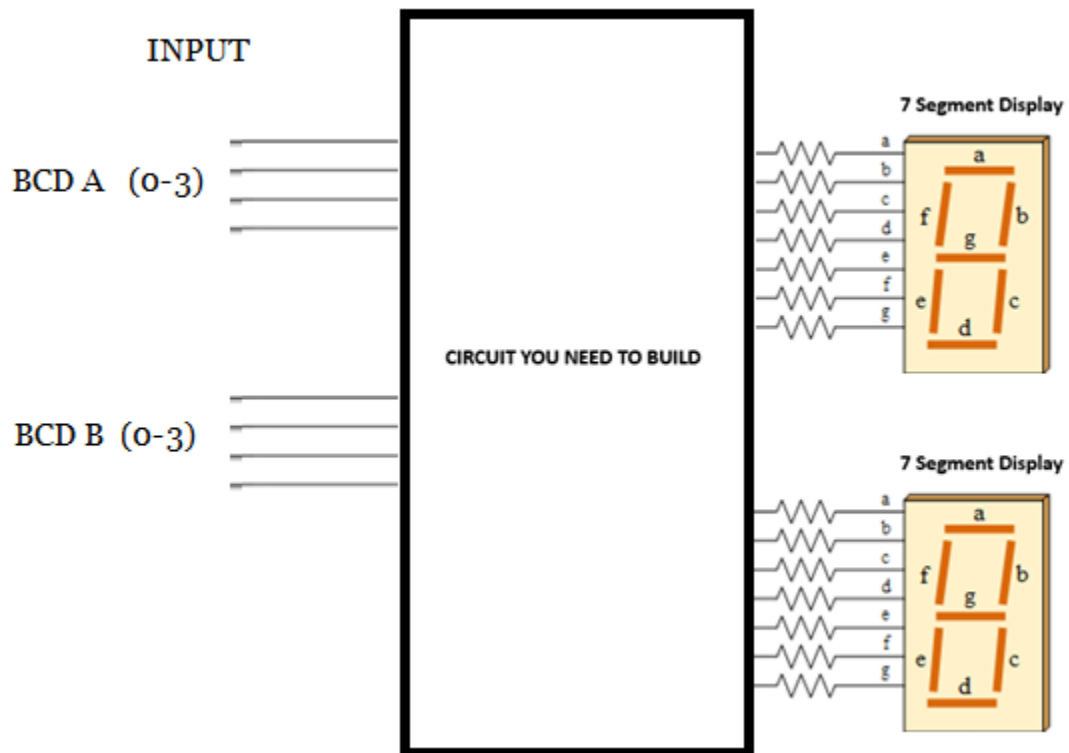


EEL 3705

Hands on Project 2

I. Implement the next circuit:




Build a BCD Adder.

Enter two valid BCD numbers. Show the result in two seven segment displays (You can use only one seven segment display and one LED for the tens value).


NEXT PAGE->

NOTE..

I won't accept anything like this:

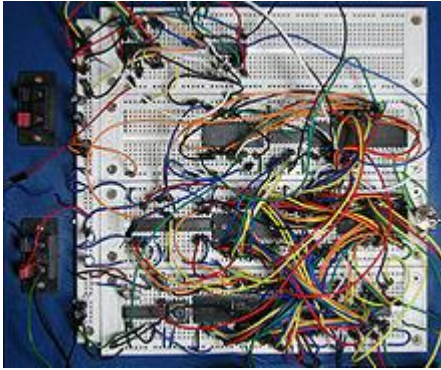

I will only accept like this

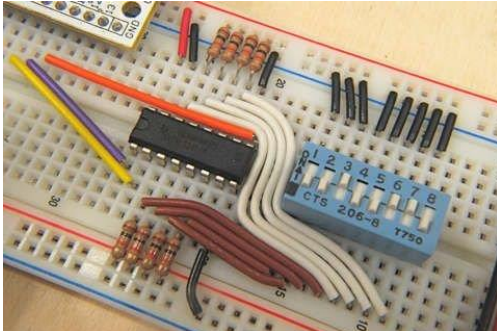

Good Luck